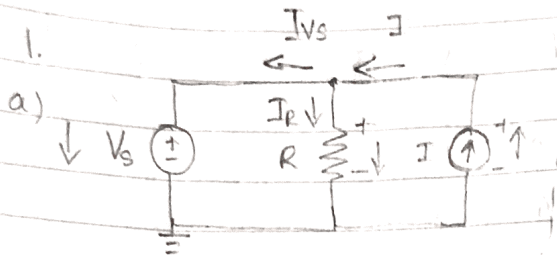


Homework 8.



$$R = 5000$$

$$I = 5 \times 10^{-3}$$

$$V_s = 5$$

$$\therefore P_{V_s} = -V_s I_{V_s}$$

$$P_R = V_s I_R$$

$$P_I = -V_s I$$

Using KCL:

$$I_{V_s} + I_R = I$$

$$I_{V_s} = I - I_R$$

$$\rightarrow \therefore I_{V_s} = I - \frac{V_s}{R}$$

$$\therefore P_{V_s} = -V_s \cdot \left(I - \frac{V_s}{R} \right)$$

$$= (-5) \left(5 \times 10^{-3} - \frac{5}{5 \times 10^3} \right)$$

$$= (-5) \left(\frac{25 - 5}{5 \times 10^3} \right)$$

$$= \frac{-100}{5 \times 10^3} = \underline{\underline{-0.02 \text{ W}}}$$

b)

$$V_s = I_R R$$

$$\therefore I_R = \frac{V_s}{R}$$

$$\therefore P_R = V_s \cdot \frac{I_R}{R}$$

$$= \frac{(V_s)^2}{R}$$

$$= \frac{25}{5 \times 10^3} = \underline{\underline{0.05 \text{ W}}}$$

$$\therefore P_I = -V_s I$$

$$= -5 \cdot (5 \times 10^{-3})$$

$$= \underline{\underline{-0.025 \text{ W}}}$$

$$c) P_J = -40 \times 10^{-3}$$

$$P_I = V_S \cdot I$$

$$-40 \times 10^{-3} = (5) I$$

$$I = -8 \times 10^{-3}$$

$$P_R = V_R I_R$$

$$= V_S \cdot \frac{V_S}{R} = \frac{5}{5 \times 10^3} =$$

$$P_{V_S} = -V_S \cdot I_{V_S} \rightarrow I_{V_S} = I - I_R$$

$$= -5 \cdot \left(I - \frac{V_S}{R} \right)$$

$$= (-5) \left((8 \times 10^{-3}) - \frac{5}{5 \times 10^3} \right)$$

$$= -0.035 \text{ W}$$

2.

a) $R_L = \infty \Rightarrow$ when $R = \infty$, the current through the resistor is 0, and so the potential difference is V_S .

$$I_L = 0$$

$$\therefore V_L = V_S$$

$$P_L = 0$$

b) To maximize current, we need resistance $R_L = 0$.

\therefore There is no difference in potential and so $V_L = 0$.

$$R_L = 0$$

$$I_L = V_S / R_S$$

$$V_L = 0$$

$$P_L = 0$$

$$c) P = VI = I^2 R = \frac{V^2}{R}$$

$$\therefore I_L = \frac{V_3}{R_S + R_L}$$

$$\therefore P = \left(\frac{V_3}{R_S + R_L} \right)^2 \cdot R_L$$

$$= \frac{(V_3)^2 \cdot R_L}{(R_S + R_L)^2}$$

$$= \frac{(100 \times 10^{-8}) \cdot R_L}{(50 + R_L)^2}$$

$$\therefore P_L = 5 \times 10^{-9} \text{ W.}$$

$$\therefore R_L = 50 \, \Omega$$

$$\therefore I = 0.00001 \text{ A.}$$

$$V_L = \frac{V_3 R_L}{R_S + R_L}$$

$$\therefore V = IR$$

$$I = \frac{V}{R}$$

$$\therefore I_L = \frac{V_L}{R_L} = \left(\frac{V_3 R_L}{R_S + R_L} \right) \frac{1}{R_L}$$

$$= \frac{V_3}{R_S + R_L}$$

$$d) 50 \, \Omega$$

8.

a) Capacity = $2770 \times 10^{-3} \text{ Ah}$
Voltage = 3.8 V .

Typical Usage = 0.3 W .

$P = VI$.

$$I = \frac{0.3}{3.8}$$

$$\therefore \text{time} = (2770 \times 10^{-3}) \cdot \frac{0.3}{3.8}$$

$$= \boxed{35.1} \text{ hours.}$$

b) $Q = 2770 \times 10^{-3} \times 3600 = 9972 \text{ As.} = 9972 \text{ C}$

$$\therefore \text{No of Electrons} = \frac{9972}{1.602 \times 10^{-19}} = \underline{6.225 \times 10^{22}}$$

c) Energy = $\text{WS} \Rightarrow \text{Power} \cdot \text{time}$.

$$\text{Energy} = (2770 \times 10^{-3}) (3.8) \times 3600$$

$$= \underline{37893.6 \text{ WS}}$$

d) $\therefore 31 \times 37893.6 \times \frac{1}{3600} \times \frac{1}{1000} \times 0.12 \approx \underline{4 \text{ cents}}$

e) $V_2 = \frac{5 \times 10^{-3}}{(201 \times 10^{-3})} = 0.02488$.

$$\therefore P = VI = \frac{V^2}{R} = \frac{(0.02488)^2}{1 \times 10^{-3}}$$

$$= \boxed{0.619} \text{ W}$$

4.

a) $R_1 = 100 \Omega$ $R_2 = 200 \Omega$

V_{out}

$$V_{out} = \frac{R_2 V_s}{R_1 + R_2} - 0$$

$$= \frac{200 \cdot 5}{100 + 200} - 0$$

$$= \underline{\underline{3.3 \text{ V}}}$$

V_{meas}

$$\frac{1}{R} = \frac{1}{R_2} + \frac{1}{R_{VM}}$$

$$\therefore R_T = \frac{1}{\left(\frac{1}{R_2} + \frac{1}{R_{VM}}\right)}$$

$$= \frac{1}{\left(\frac{1}{200} + \frac{1}{1 \times 10^6}\right)} = \underline{\underline{199.96}}$$

$$\therefore V_{meas} = \frac{R_T V_s}{R_1 + R_T} - 0$$

$$= \frac{(199.96)(5)}{100 + 199.96} = \underline{\underline{3.33311}}$$

b) $V_{out} = \frac{(10 \times 10^6) \cdot 5}{20 \times 10^6} = \underline{\underline{2.5 \text{ V}}}$

$$R_T = \frac{1}{\left(\frac{1}{10 \times 10^6} + \frac{1}{1 \times 10^6}\right)} = 909090.9091 \quad \therefore V_{meas} = \underline{\underline{0.416 \text{ V}}}$$

\therefore This voltmeter is not good.

7. I worked on Q1, Q2 during Homework Party on Thursday and Q3, Q4 during office hours on Friday. I worked with the people in office hours.